

CPE201


Digital Design

By Benjamin Haas


Class 7: PLDs, Boolean Laws, and Equipment



PLDs

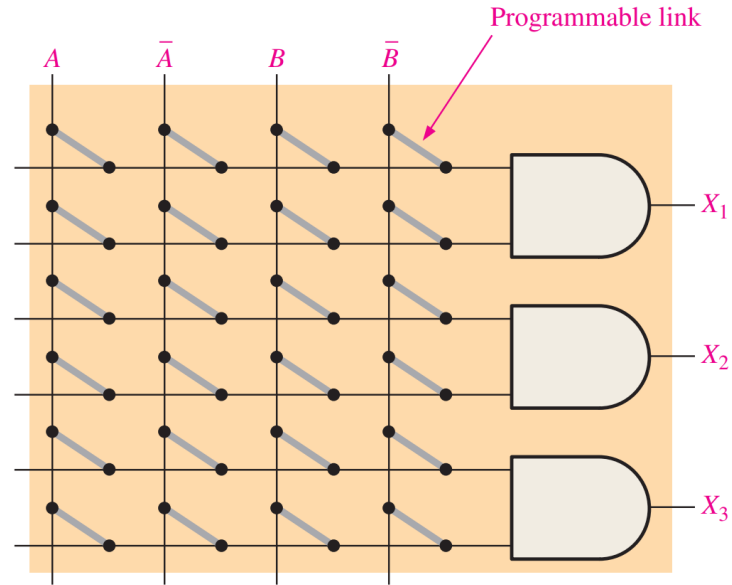

(a) Unprogrammed


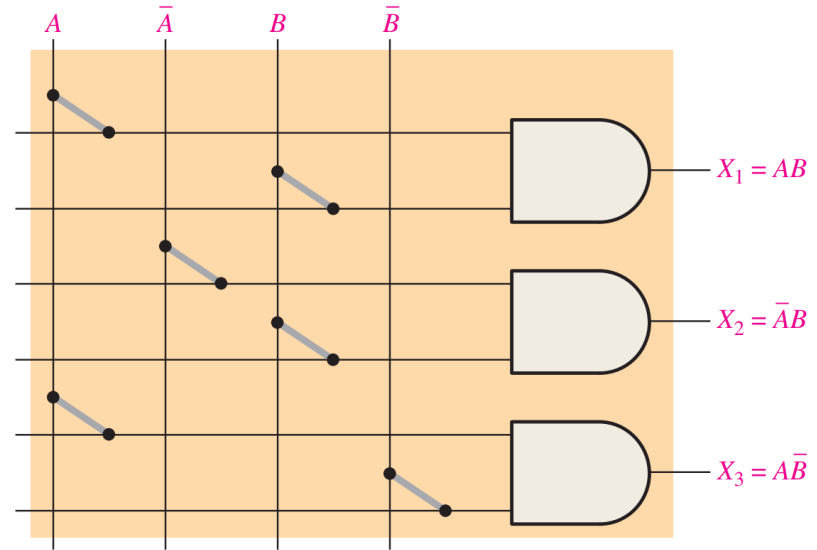


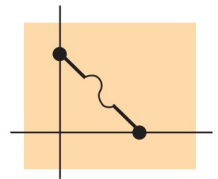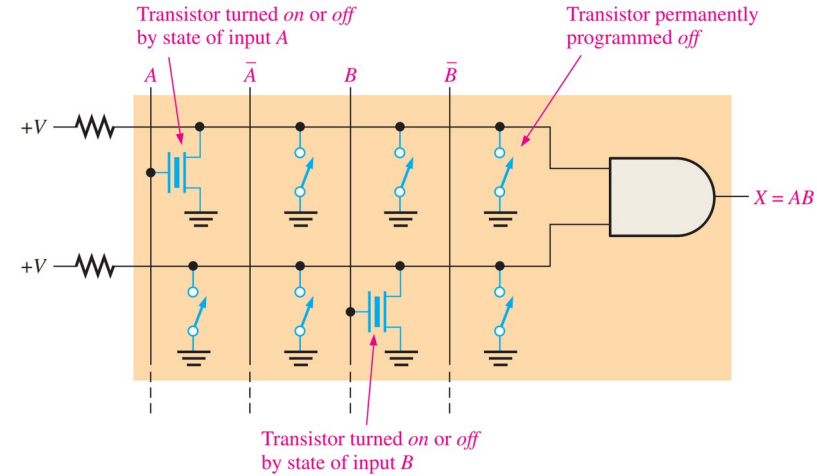(b) Programmed




OTPs


- One Time Programmable
- Many types
- Burn it out!




(a) Fuse intact before programming

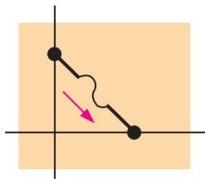


(b) Programming current

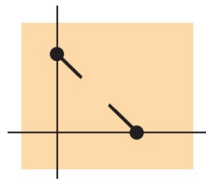


(c) Fuse open after programming

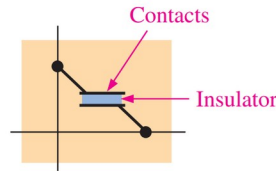

(a) Antifuse is open before programming.

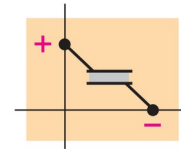

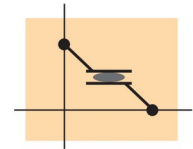(b) Programming voltage breaks down insulation layer to create contact.




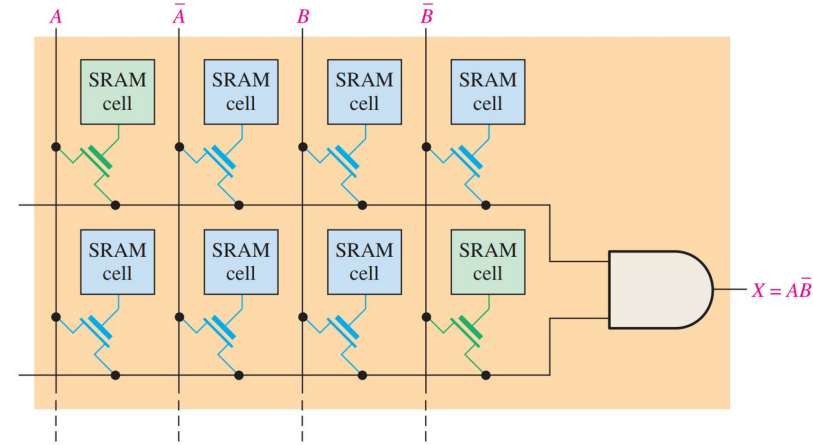(c) Antifuse is effectively shorted after programming.




Reprogrammable


- Different tech
- Different cost
 - More circuitry



(a) SRAM-based programmable array

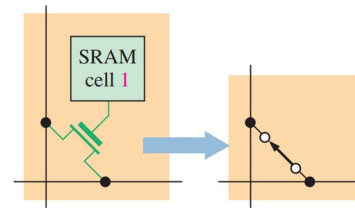

(b) Transistor *on*


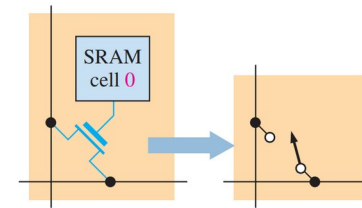


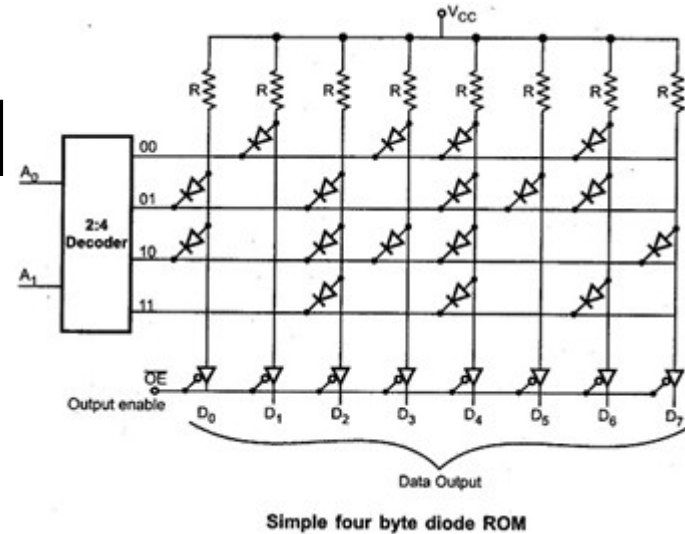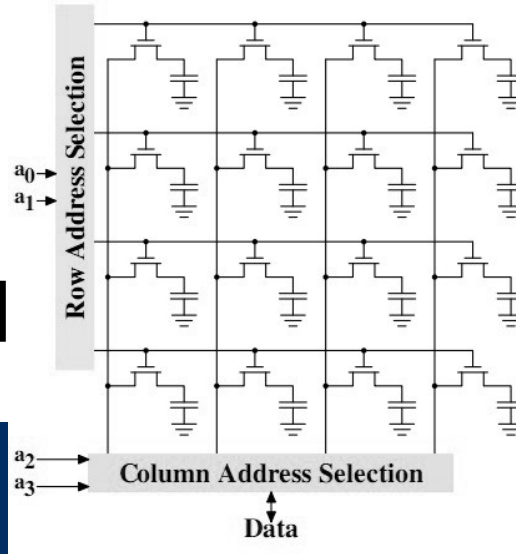(c) Transistor *off*



ROM/RAM

- Same concept as PLD
- Address lines in
- Stores data
- RAM vs ROM



Programming




Tape-out and Packing Handler



Programming/Debugging

- Development
- In-system
 - JTAG
 - SWD

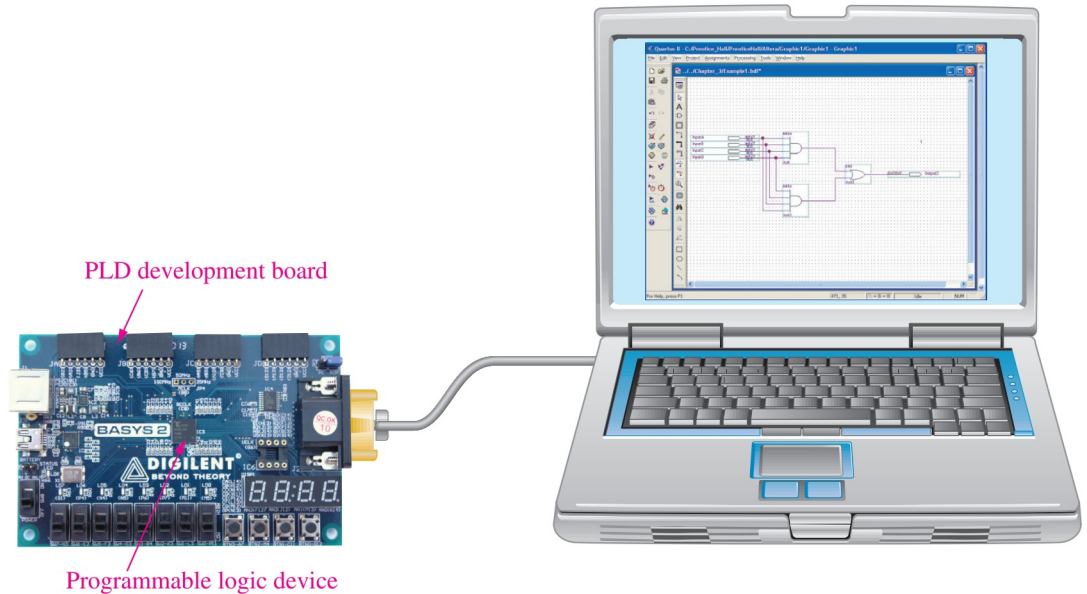

Boolean Addition

Truth tables:

- Same as OR
 - Remember that here 0=FALSE, 1=TRUE

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0



Boolean Multiplication

- Same as AND

Truth tables:

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0




Boolean Laws

- Commutative Laws
- Associative Laws
- Distributive Laws
- 12 Rules for Simplification
- Why?
 - Not every system has these laws, i.e. matrices




Commutative Laws

- $A + B = B + A$

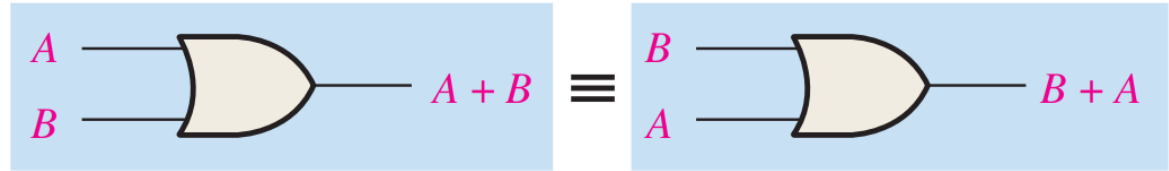


- $AB = BA$

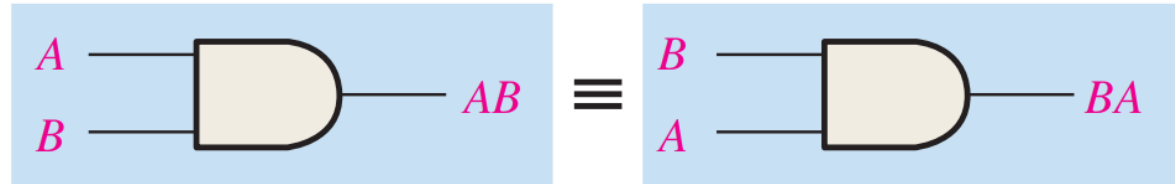


Associative Laws

- $A + (B + C) = (A + B) + C$

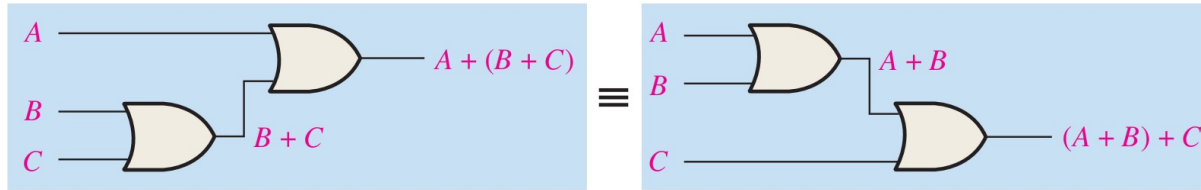


- $A(BC) = (AB)C$

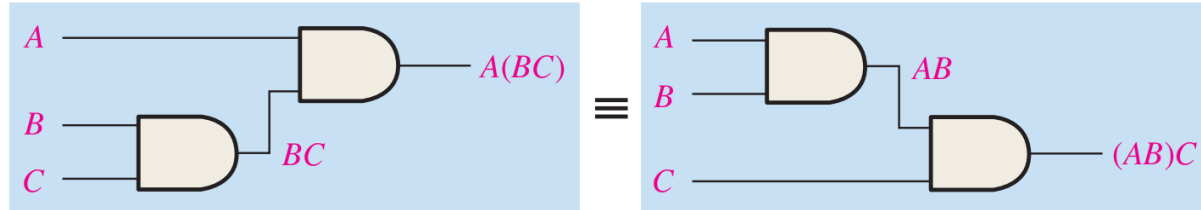

Distributive Laws

- $A(B + C) = AB + AC$

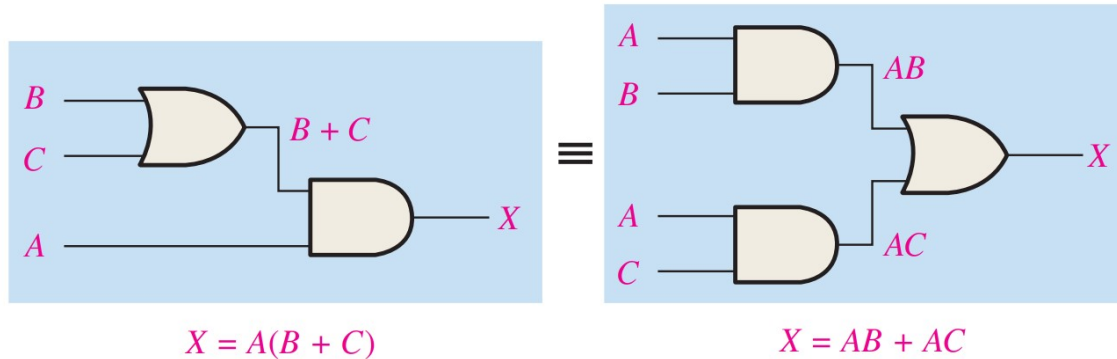

12 Rules for Simplification

- 1. $A + 0 = A$



- 2. $A + 1 = 1$



12 Rules for Simplification

- 3. $A \cdot 0 = 0$





- 4. $A \cdot 1 = A$





12 Rules for Simplification

- 5. $A + A = A$

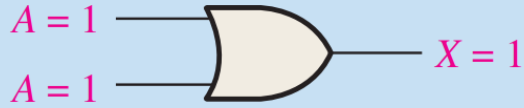
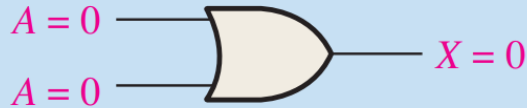


- 6. $A + A' = 1$

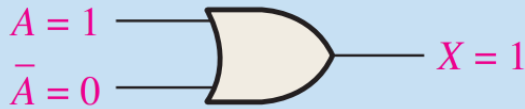
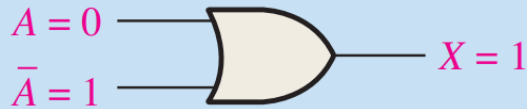


12 Rules for Simplification

- 7. $A \cdot A = A$

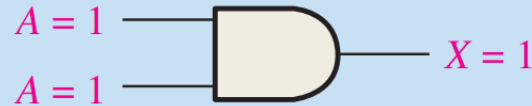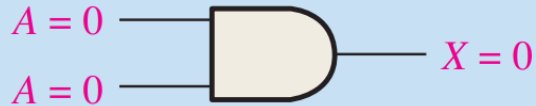


- 8. $A \cdot A' = 0$

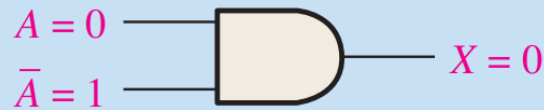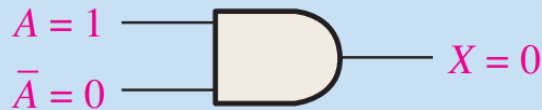

12 Rules for Simplification


- 9. $A'' = A$

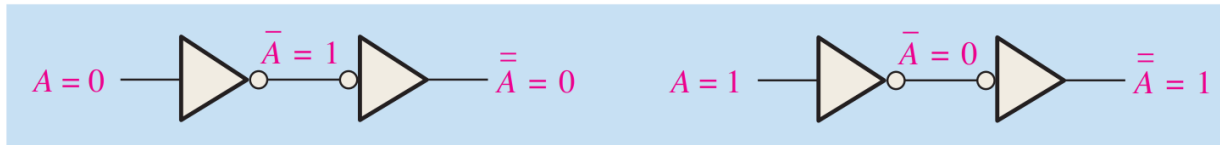

- 10. $A + AB = A$

A	B	AB	$A + AB$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1


↑ equal ↑

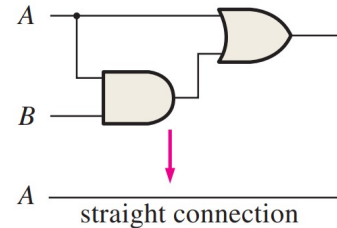

12 Rules for Simplification

- 11. $A + A'B = A + B$

A	B	$\bar{A}B$	$A + \bar{A}B$	$A + B$
0	0	0	0	0
0	1	1	1	1
1	0	0	1	1
1	1	0	1	1

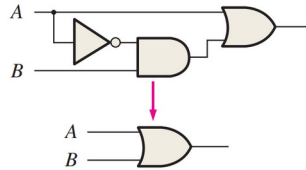

↑ equal ↑

- 12. $(A + B)(A + C) = A + BC$

- Also follows from distribution, Rule 7, and Rule 10
- Diagram in book



Equipment

- Test and debugging equipment
- Debugging origin
 - Literal bugs



Multimeter

- Your best friend!
 - Voltage
 - Current
 - Resistance
 - Continuity



(a) Bench-type DMM



(b) Handheld DMM



Oscilloscope

- Oscoppe or scope
 - Measures and displays signals
- The fastest ADC you'll typically use




Oscope




Oscope

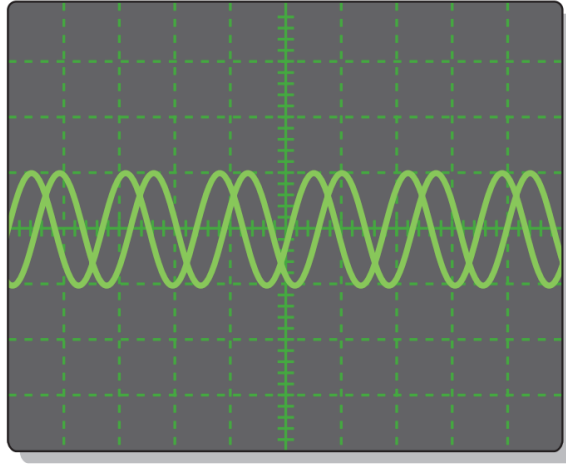- Vertical and Horizontal controls
- Triggers



(a) Untriggered waveform display

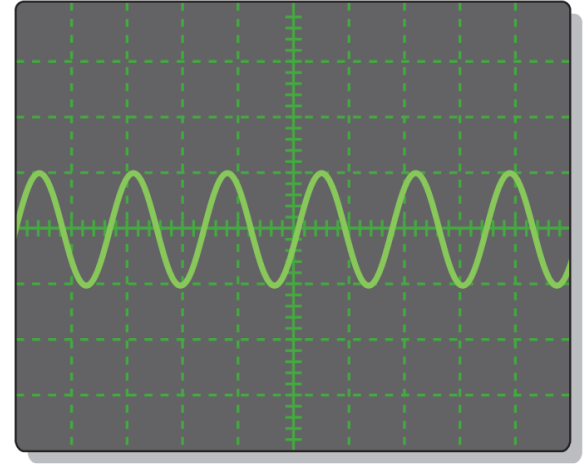


(b) Triggered waveform display




Oscope

- AC vs DC coupling

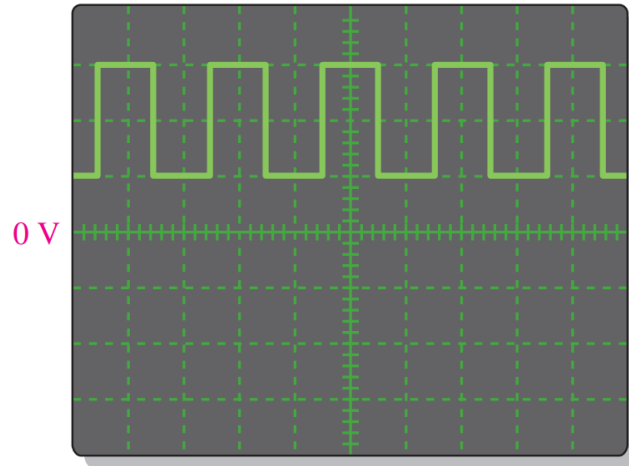

(a) DC coupled waveform

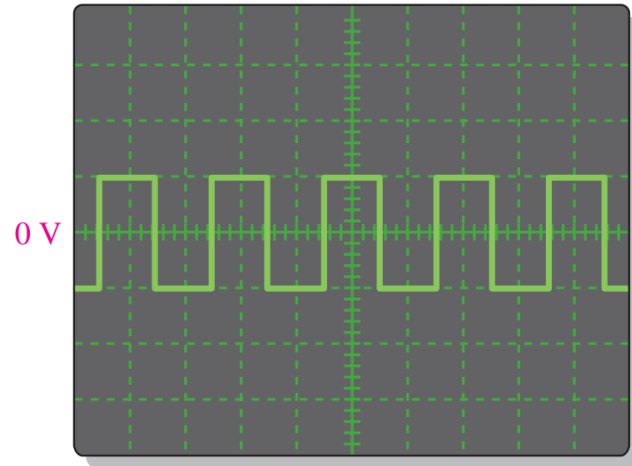


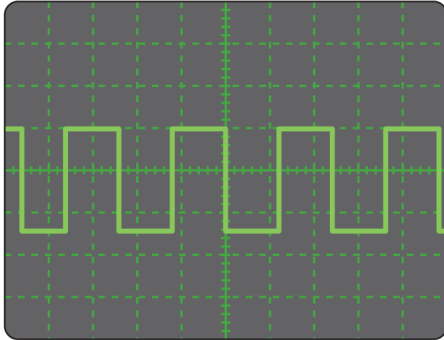(b) AC coupled waveform




Oscope


- Compensation and Loading
- Shopping cart example



Properly compensated

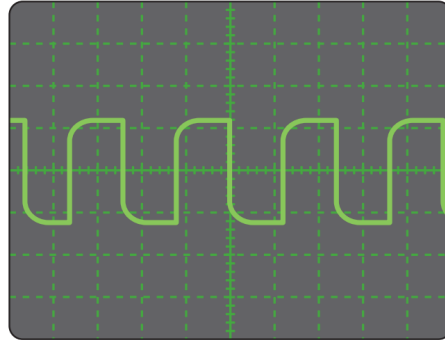

Undercompensated

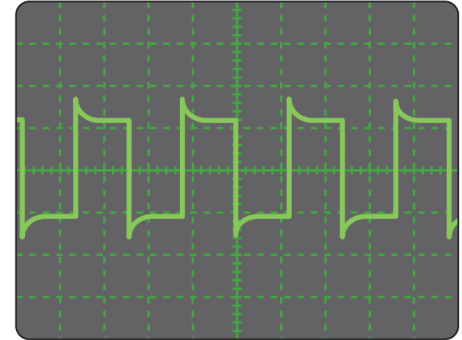

Overcompensated



Probes

Voltage



Current



Multi



Power Supply

- DC Voltages
 - Circuit power
 - Very stable




Generators

- Arbitrary vs Function



Logic Analyzer

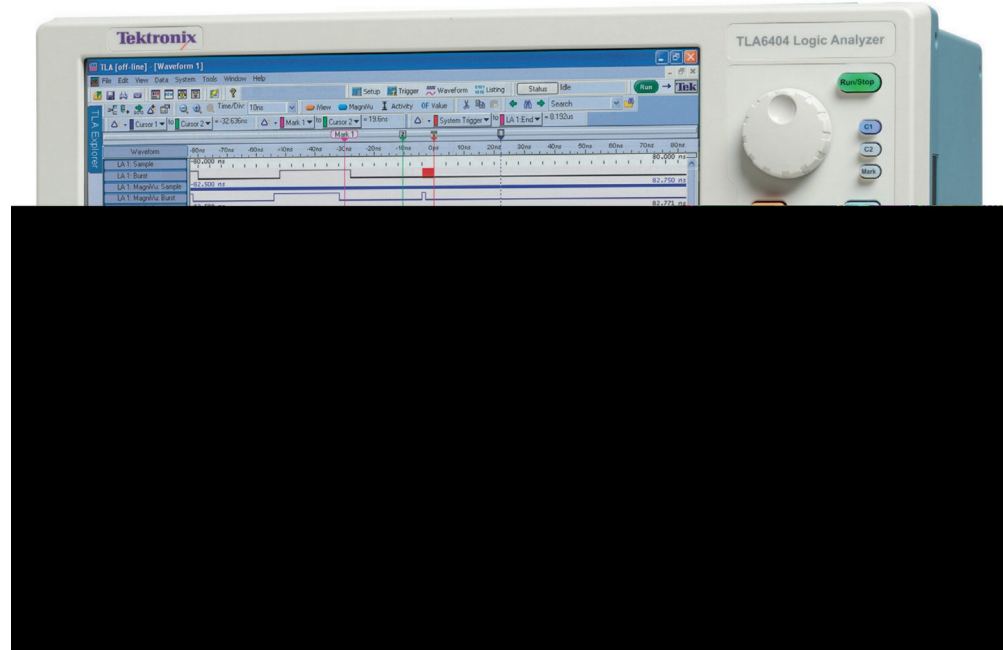- Oscilloscope+
- Can measure
 - And decode!
- Costs extra



Others

- Frequency Analyzer
- RLC meters
- Fiber optics
- Anything you could want, pretty much



Reading

- This lecture
 - Sections 3.7, 1.7, 4.1-4.2
- Next lecture
 - Sections 4.3-4.6

