

# CPE201

# Digital Design

By Benjamin Haas

Class 18: Flip-Flops







# Vocabulary

- Bistable Multivibrator
  - 2 States
- Synchronous
  - There is a clock
- Clock
  - Signal that alternates H/L at a set interval


    
# Vocab

- Edge Triggered
  - State changes on edge
  - Positive or rising edge
  - Negative or falling edge




D


J-K



# D Flip-Flop

 

 (a)  $D = 1$  flip-flop SETS on positive clock edge. (If already SET, it remains SET.)




(b)  $D = 0$  flip-flop RESETS on positive clock edge. (If already RESET, it remains RESET.)

Truth table for a positive edge-triggered D flip-flop.




Inputs		Outputs		Comments
$D$	CLK	$Q$	$\bar{Q}$	
0	↑	0	1	RESET
1	↑	1	0	SET

↑ = clock transition LOW to HIGH

# Example

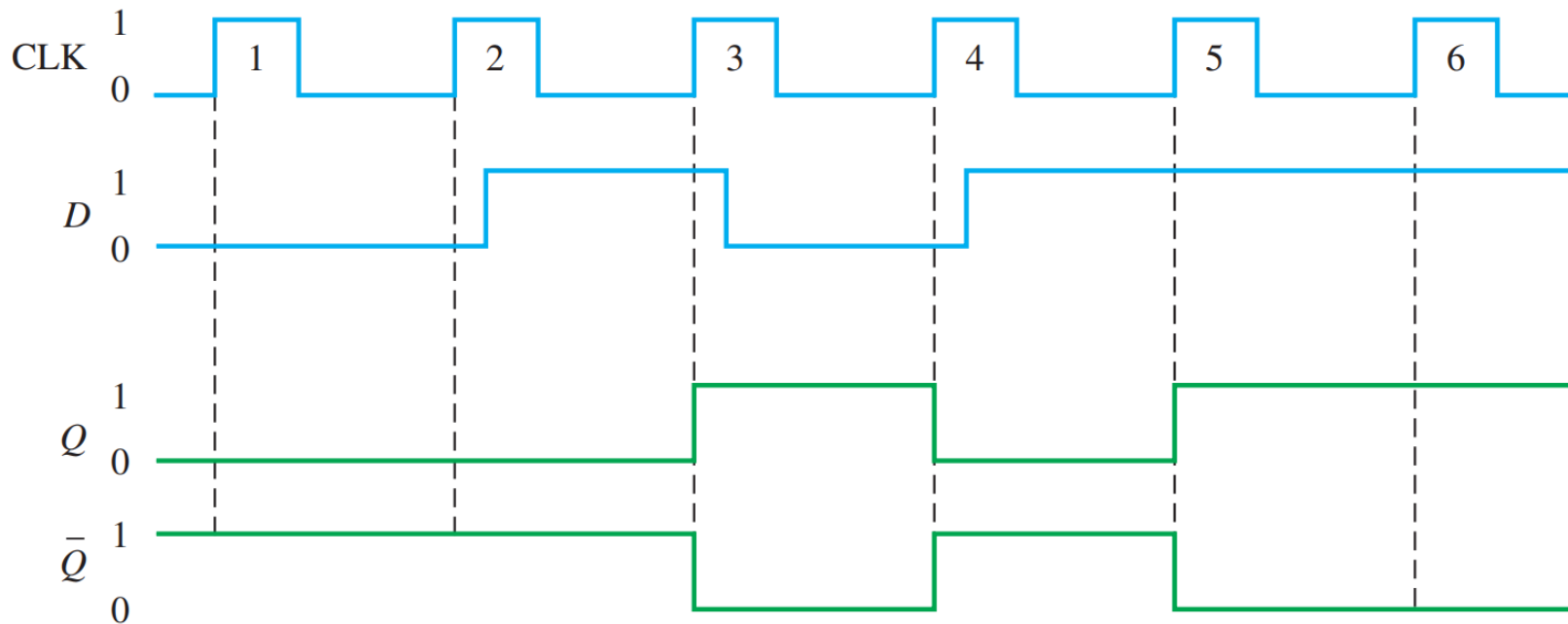


# Edge Detection

   

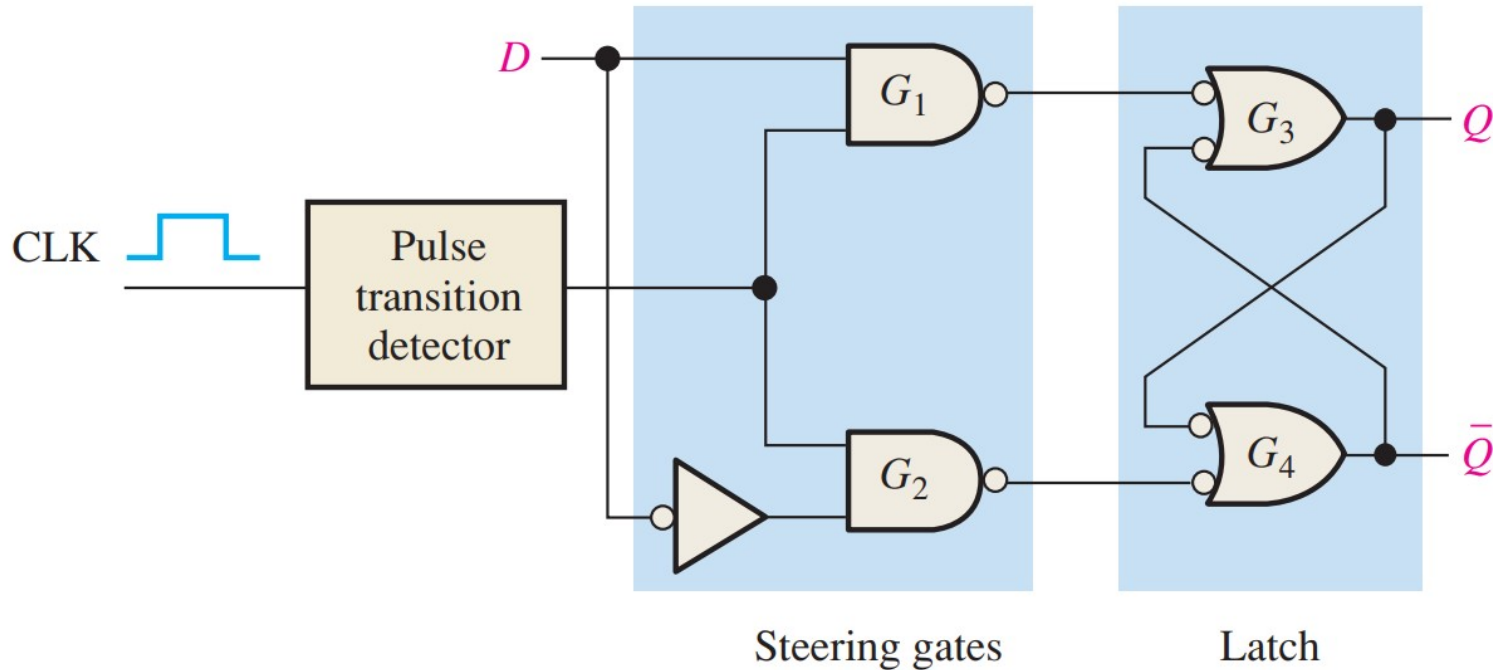
# Circuit

- $G_3$  and  $G_4$  are NANDs (like from latches)



# Circuit Walkthrough

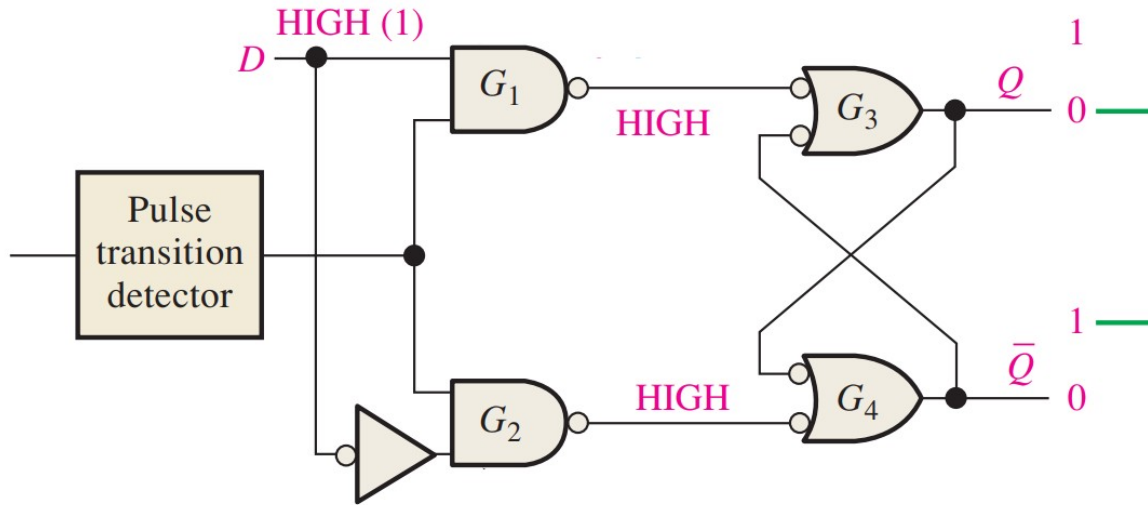

Truth table for a 2-input NAND gate.

Inputs		Output
$A$	$B$	$X$
0	0	1
0	1	1
1	0	1
1	1	0





# J-K Flip-Flop


- S-R Latch+

Truth table for a positive edge-triggered J-K flip-flop


Inputs			Outputs		Comments
$J$	$K$	CLK	$Q$	$\bar{Q}$	
0	0	↑	$Q_0$	$\bar{Q}_0$	No change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	$\bar{Q}_0$	$Q_0$	Toggle

↑ = clock transition LOW to HIGH  
 $Q_0$  = output level prior to clock transition

# Example

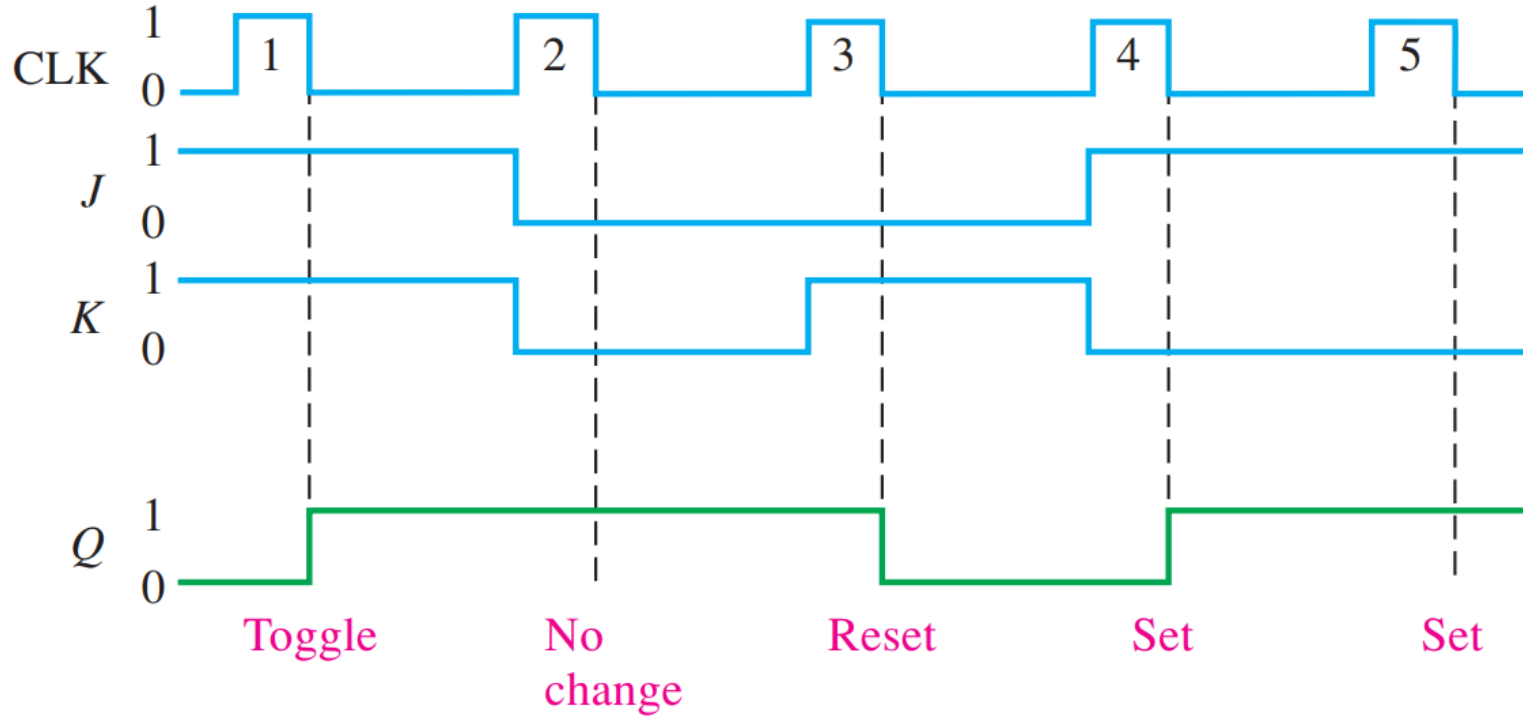

# Circuit

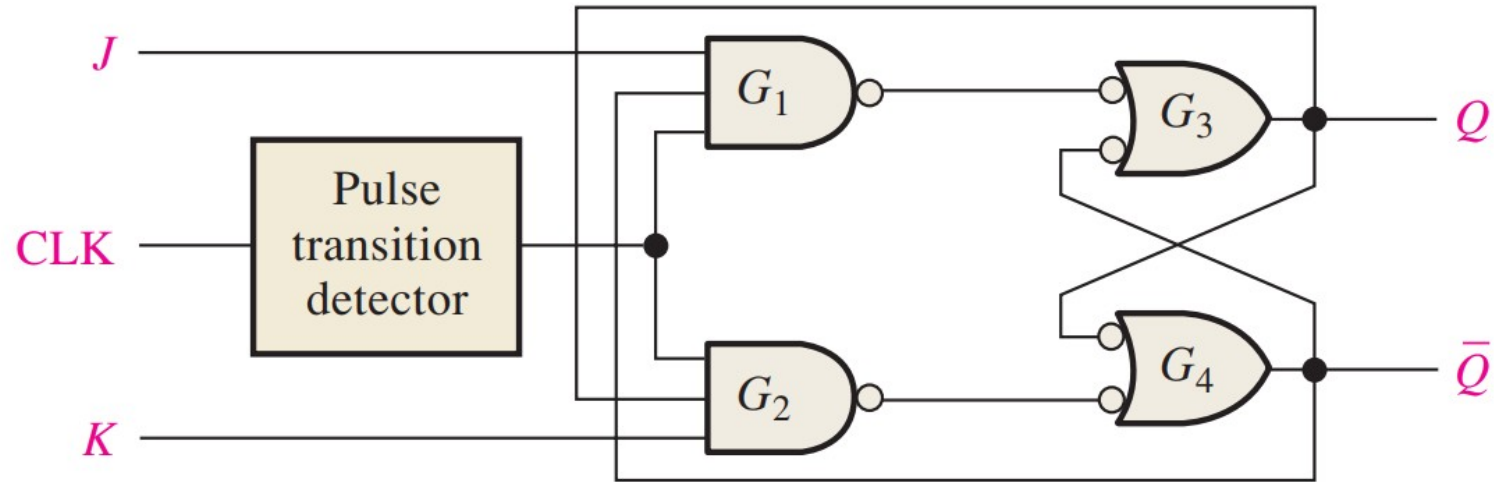


# Asynchronous Set and Reset

- Independent on clock
  - Initialization on startup
  - Override
- Also called Preset and Clear



# Circuit

 


# Preset and Clear

- Reaches into the Latch portion of the circuit
- Can also be done in J-K Flip-Flop
- Active Low inputs
  - Normal operation is both high
  - Both low creates latch invalid state





# Example

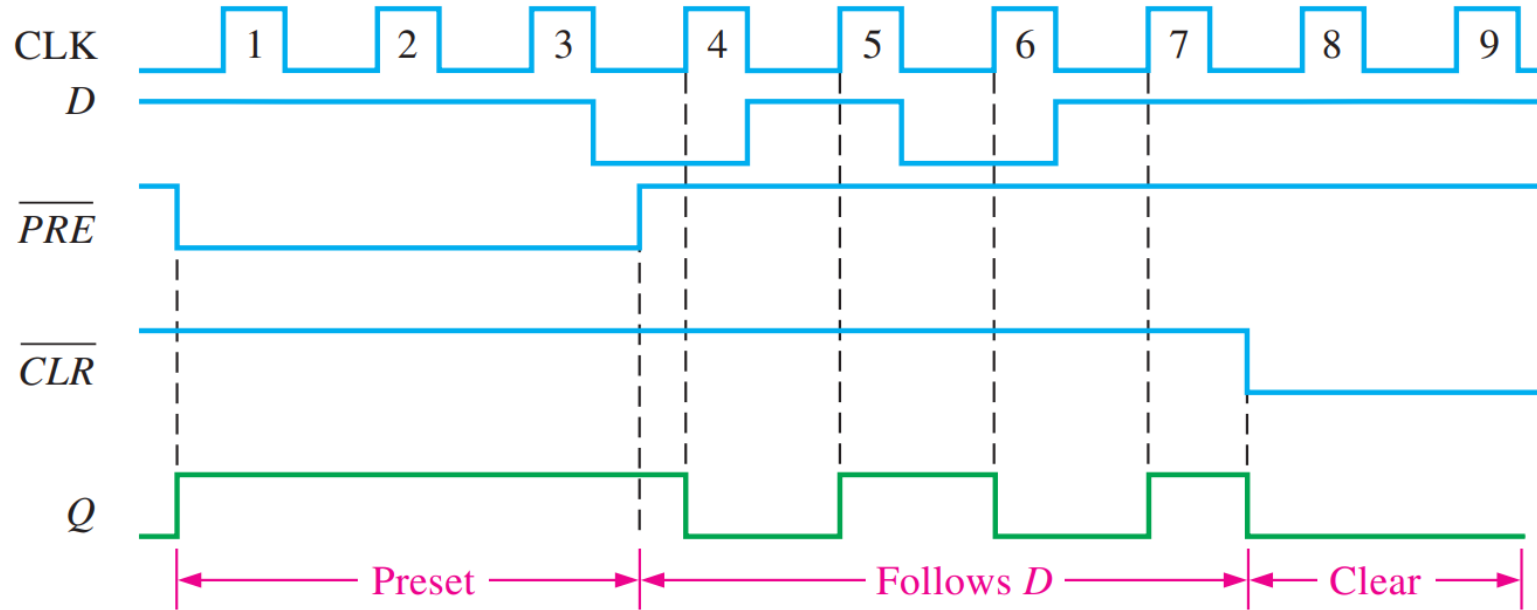
  
# Application – Data Storage



- Parallel storage
- Data on lines stored at each clock
- Covered more later





  
# Application - Frequency Division

- Divide by 2
- Good for running multiple subsystems



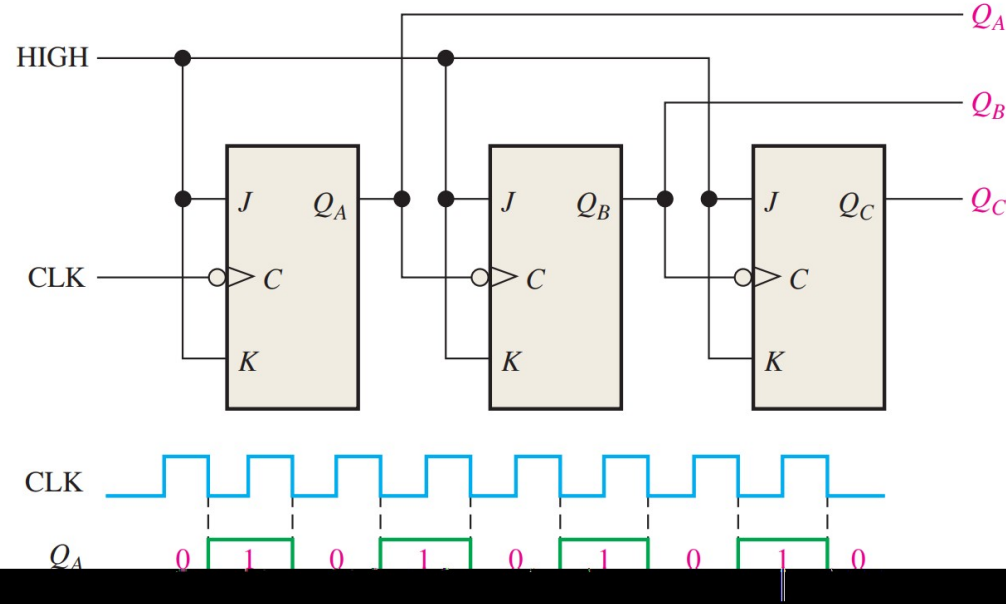
# Application - Counting

- Like freq division
- Line up the divisors to count in binary
- Counts clock cycle
- J-Ks instead of Ds




# Real Chips – 74HC74 and


## 74HC112

 


Individual logic symbols

 

 Single block logic symbol  
Note: The S and R inside the block indicate that  $\overline{PRE}$  SETS and  $\overline{CLR}$  RESETS.




Individual logic symbols

 

Single block logic symbol


The 74HC112 dual negative edge-triggered J-K flip-flop.

# Propagation Delays

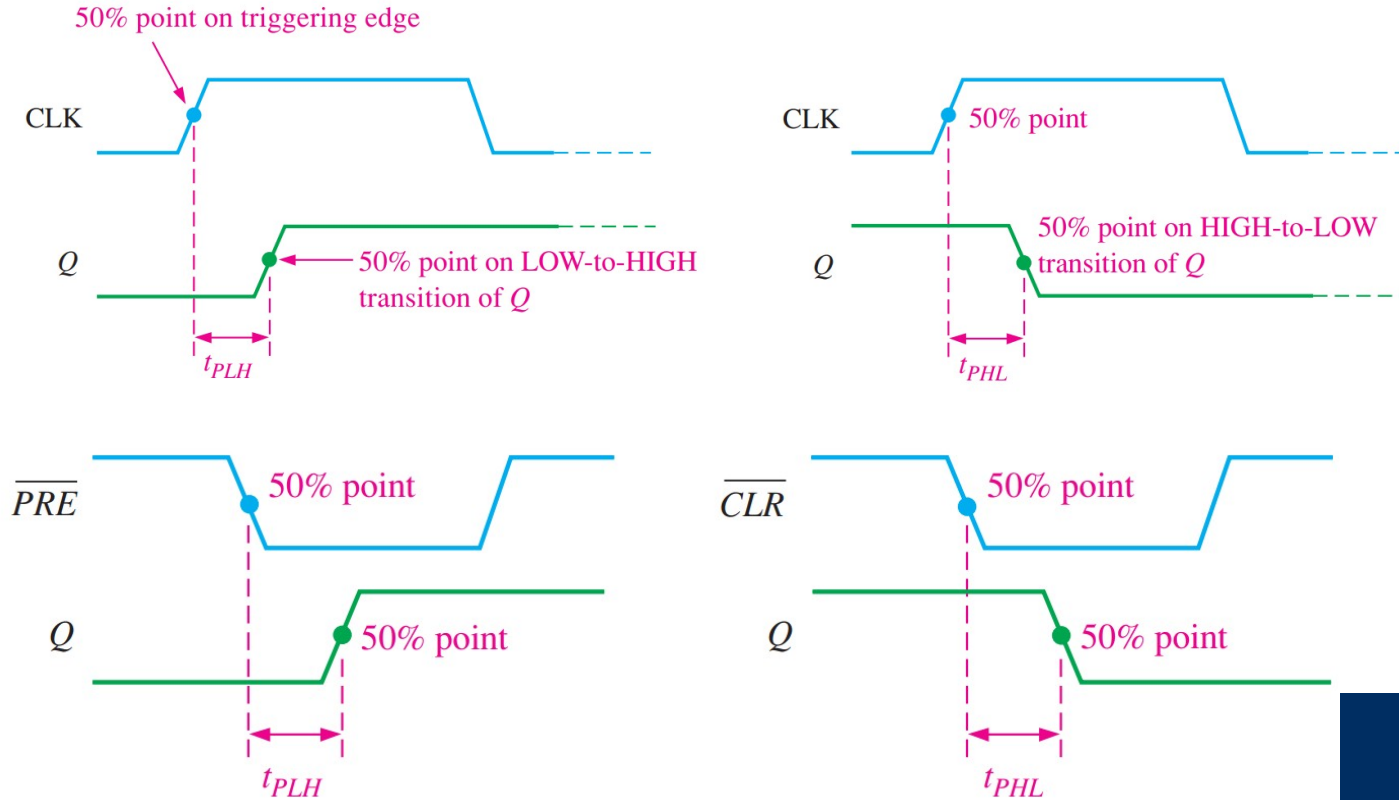

 
# Setup Time

- Data time on the line BEFORE clocking it in


 
# Hold Time

- Data time on the line AFTER clocking it in



# Reading

- This lecture
  - Sections 7.2-7.4
- Next lecture
  - Sections 7.5-7.7

