

Answer all questions completely. Put a box around the final solution. Put your name on it. Show your work.

By hand:

- Given the waveforms in Figure 1, design a circuit that will generate the output waveform given the input waveforms.

 


Figure 1

There are several ways to tackle this. You could look at the inputs and try to come up with an output. I'm going to make a truth table of the inputs and then use a Karnaugh map to minimize the circuit logic.

The truth table can be created by looking for a place in the signal that has the inputs matching each row of the truth table and then recording what the output is at that point.

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1


Putting this truth table into a Karnaugh map and making groupings of 1's gives:

AB	C	0	1
00	0	0	
01	0	0	
11	0	1	
10	1	1	

Then the minimized output expression is:

$$\text{Output} = AB' + AC$$

Writing this as a circuit gives:

 

- Given the Boolean expression $X = A'(B + C'(D' + E))$, give the SOP circuit that implements the minimized expression.

We need to fully distribute,

$$X = A'(B + C'(D' + E))$$

$$X = A'(B + C'D' + C'E)$$

$$X = A'B + A'C'D' + A'C'E$$


This expression is in SOP form. Making a Karnaugh map to see if it minimized:

		E'				
		CD	00	01	11	10
AB	00	1	0	0	0	0
	01	1	1	1	1	1
11	0	0	0	0	0	0
10	0	0	0	0	0	0

		E				
		CD	00	01	11	10
AB	00	1	1	0	0	0
	01	1	1	1	1	1
11	0	0	0	0	0	0
10	0	0	0	0	0	0

The three groupings are in different colors for readability. They are the original terms $A'B + A'C'D' + A'C'E$

 This expression is minimized, so we can create the SOP circuit:



3. Given the following inputs, give the outputs for a full adder.

We can use the truth table for a full adder to get these answers

a. $A = 1, B = 0, \text{Cin} = 0$

$$\Sigma = 1$$

$$C_{\text{out}} = 0$$

b. $A = 1, B = 1, \text{Cin} = 1$

$$\Sigma = 1$$

$$C_{\text{out}} = 1$$

c. $A = 0, B = 0, \text{Cin} = 1$

$$\Sigma = 1$$

$$C_{\text{out}} = 0$$

4. Given the 5-bit parallel adder circuit in Figure 2 and the following input sequences, determine the sum outputs of the 5-bit parallel adder after each input set (i.e. $A_0 = 1, A_1 = 0$, etc. then $A_0 = 0, A_1 = 1$, etc.)

$$A_0 \quad 1010$$

$$A_1 \quad 0110$$

$$A_2 \quad 1110$$

$$A_3 \quad 1010$$

$$A_4 \quad 0100$$

$$B_0 \quad 0001$$

$$B_1 \quad 1111$$

$$B_2 \quad 1011$$

$$B_3 \quad 0011$$

$$B_4 \quad 0101$$

 


Figure 2

Each set of outputs can be made from the truth table of a full adder.

At t=1, the inputs from left to right are:

A ₄	B ₄	A ₃	B ₃	A ₂	B ₂	A ₁	B ₁	A ₀	B ₀
0	0	1	0	1	1	0	1	1	0

The carry bits from left to right are:

Cout4	Cout3	Cout2	Cout1	Cout0
0	1	1	0	0

Then the outputs for t=1 from left to right are:

Σ_6	Σ_5	Σ_4	Σ_3	Σ_2	Σ_1
0	1	0	0	1	1

At t=2, the inputs from left to right are:

A_4	B_4	A_3	B_3	A_2	B_2	A_1	B_1	A_0	B_0
1	1	0	0	1	0	1	1	0	0

The carry bits from left to right are:

Cout4	Cout3	Cout2	Cout1	Cout0
1	0	1	1	0

Then the outputs for t=2 from left to right are:

Σ_6	Σ_5	Σ_4	Σ_3	Σ_2	Σ_1
1	0	1	0	0	0

At t=3, the inputs from left to right are:

A_4	B_4	A_3	B_3	A_2	B_2	A_1	B_1	A_0	B_0
0	0	1	1	1	1	1	1	1	0

The carry bits from left to right are:

Cout4	Cout3	Cout2	Cout1	Cout0
0	1	1	1	0

Then the outputs for t=3 from left to right are:

Σ_6	Σ_5	Σ_4	Σ_3	Σ_2	Σ_1
0	1	1	1	0	1

At t=4, the inputs from left to right are:

A_4	B_4	A_3	B_3	A_2	B_2	A_1	B_1	A_0	B_0
0	1	0	1	0	1	0	1	0	1

The carry bits from left to right are:

Cout4	Cout3	Cout2	Cout1	Cout0
0	0	0	0	0

Then the outputs for t=4 from left to right are:

Σ_6	Σ_5	Σ_4	Σ_3	Σ_2	Σ_1
0	1	1	1	1	1