

CPE201

Digital Design

By Benjamin Haas

Class 24: Counters, Design and Applications



University of Nevada, Reno


Outline

- Cascading Counters
- Counter Decoding
- Counter Applications



Asynchronous Cascading

 - Asynchronous is a simple cascade
 - Be wary of the time for ripple to complete




Synchronous Cascading

- Synchronous uses chip features
 - Count Enable (CTEN)
 - Lets the counter run
 - Terminal Count (TC)
 - A pulse every time the counter rolls over




Synchronous Cascading

 - Counter 2 goes up one count every time Counter 1 rolls over
 - Frequency Divider




Cascading

 - Multiply the mod counts to get the total
 - Can also make multiple clock frequencies




Truncated Cascading

 - Use loading capability to change start value
 - Ex start at 0x63C0 = 25,536 out of





Counter Decoder

 - Simple decoder
 - A pulse when the counter has a certain value
 - After data bits in a U




Avoid Glitches

  - Sample only when the data is ready, not continuously



Strobe Inputs

- Same concept as with MUX/DEMUX

 


Applications



- Digital Clock
- Car Parking Spot Indicator
- Serial to Parallel Conversion





Digital Clock

 



Car Parking Spot Indicator

  

Parallel to Serial

  

Troubleshooting

  


Troubleshooting

$$f_{\text{out}} = \frac{f_{\text{in}}}{\text{modulus}} = \frac{1 \text{ MHz}}{7232} \cong 138 \text{ Hz}$$

- Open can change the output frequency
 - In this chip, open acts like a high input
 
$$f_{\text{out}} = \frac{f_{\text{in}}}{\text{modulus}} = \frac{1 \text{ MHz}}{40,000} = 25 \text{ Hz}$$



Reading

- This lecture
 - Sections 9.6-9.10
- Next lecture
 - 9.5, Ch7 and Ch8 Applied Logic

