

CPE201

Digital Design

By Benjamin Haas

Class 8: DeMorgan's and Boolean Simplification



Mastery

- First submission
 - You can get between 0% and 100% for HW total
 - Correct problems – full credit, no change on resubmission
 - Incorrect problems – no credit, can be corrected in resubmission
- Second submission
 - Submit corrected work
 - Must include a reflection to change a 0% to 100%
 - Why did you get it wrong the first time and what did you learn to correct the error
 - Full sentences




Test


- Next Wednesday – 02/23
- In class
- Turn in paper submissions
- All material through this week is fair game
- 1 handwritten cheat sheet, both sides
- Calculator



NAND and NOR Equivalents

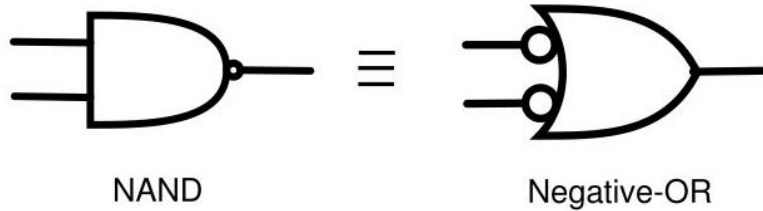

A	B	A NAND B
0	0	1
0	1	1
1	0	1
1	1	0

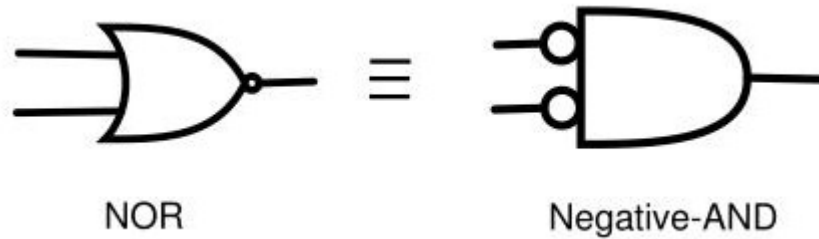

A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

- Foreshadowing...



DeMorgan's Theorem

- The mathematical equivalent
- $(XY)' = X' + Y'$
- $(X + Y)' = X'Y'$



Examples

- $(XYZ)'$
- $(X' + Y' + Z')'$
- $(W'X + Y'Z')'$
- $((A' + B') + C')'$
- $(A'B(C + D') + E)'$



DeMorgan's and XOR


- Substitution required
- $B = AB' + A'B$
- Using the Laws and 12 Rules
- $XNOR = (B)' = A'B' + AB$

A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0



Analysis of Circuits

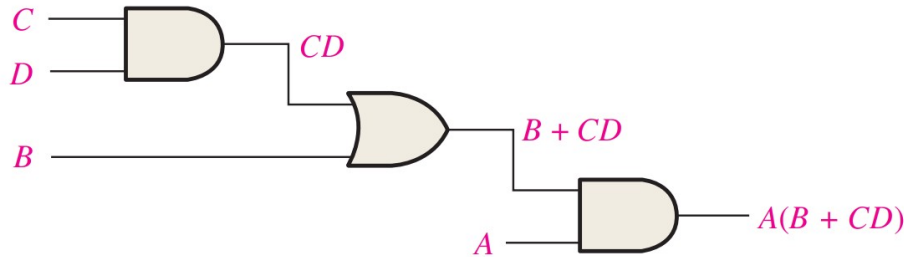- Start at the left and work right
 - (Beginning to end of circuit)
- Carry a logical output forward as an



Analysis of Circuits

- Make a truth table
 - $2^{\text{\#inputs}}$ is how many rows there are

A	B	C	D	CD	B+CD	A(B+CD)
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	1	1	0
0	1	0	0	0	1	0
0	1	0	1	0	1	0
0	1	1	0	0	1	0
0	1	1	1	1	1	0

A	B	C	D	CD	B+CD	A(B+CD)
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	0	0	0
1	0	1	1	1	1	1
1	1	0	0	0	1	1
1	1	0	1	0	1	1
1	1	1	0	0	1	1
1	1	1	1	1	1	1

Simplification

- Boolean Algebra
- Karnaugh Maps



Boolean Algebra

- Simplify expressions using the laws and 12 rules
 - Group terms together that have common terms
 - Simplify negations using DeMorgan's
 - Remove un-needed terms using the rules
 - $A + 0 = A$, $A \cdot 1 = A$, etc.




Examples

- $A'BC + AB'C' + A'B'C' + AB'C + ABC$
- $(AB)' + (AC)' + A'B'C'$
- $A + AB + AB'C$




Standard Forms

- Sum-of-products (SOP)

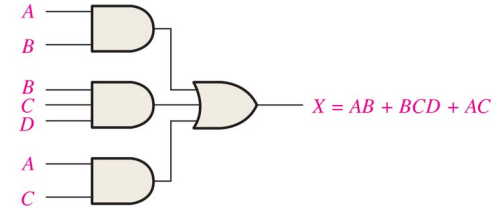

- Product-of-sums (POS)

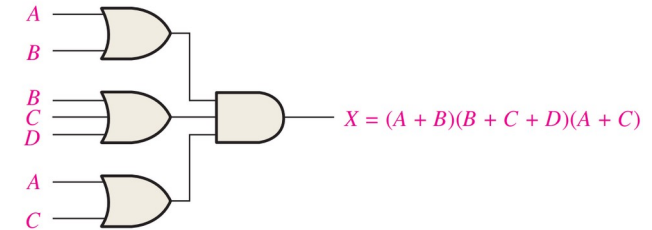

- Standard forms makes things easier



SOP

- All terms have + or • between them and no ()
- $AB + AC + ABC$ ✓
- $A'B + AC + A'B'C'$ ✗
- $A(B + C) + AB$ ✗
- $(AB)' + AC$



Making SOP

- Distribute and DeMorgan's
- $A(B + C) + AB = AB + AC$ ✓
- $(AB)' + AC = A' + B' + AC$ ✓



Standard SOP

- All inputs need to be in each product term

- $A'BC + AB'C + A'B'C$  

- $ABC + AB + A'BC'$



Expanding SOP to Standard SOP

- Use Rule 6: $A + A' = 1$
- Multiply terms by the missing variable using Rule 6 and expand
- $A'BC + AB + A'BC'$
- $AB(C + C') = ABC + ABC'$
- $A'BC + ABC + ABC' + A'BC'$



Why?

- Each term in the final expression is a line in the truth table for a 1
- You could read the truth table from the expression
- $A'BC + ABC + ABC' + A'BC' = 0'11 + 111 + 110' + 0'10'$





Example

- $AB + AB'CD$
- Expand twice



POS

- All terms are groupings of +, multiplied together
- Not can only apply to one input term at a time
- $(A' + B)(A + B + C')(A)$  
- $(A + B)'(AB + C)$



Making POS

- Use DeMorgan's and Rule 12: $(A + B)(A + C) = A + BC$
- $(A + B)' = A'B' = (A')(B')$ ✓
- $(AB + C) = (A + C)(B + C)$ ✓



Standard POS

- All inputs need to be in each sum term
- $(A' + B + C)(A + B' + C)(A' + B' + C)$ ✓
- $(A + B + C)(A + B)(A' + B + C')$ ✗



Expanding POS to Standard POS

- Use Rule 8: $A \bullet A' = 0$ to add terms
- Expand using Rule 12
- $(A' + B + C)(A + B)(A' + B + C')$
- $(A + B + CC') = (A + B + C)(A + B + C')$
- $(A' + B + C)(A + B + C)(A + B + C')(A' + B + C')$



Why?

- Each term in the final expression is a line in the truth table for a 0
- You could read the truth table from the expression
- $(A' + B + C)(A + B + C)(A + B + C')(A' + B + C') = (1' + 0 + 0)(0 + 0 + 0)(0 + 0 + 1')(1' + 0 + 1')$



Example

- $(A + B)(A + B' + C + D)$
- Expand twice



Reading

- This lecture
 - Sections 4.3-4.6
- Next lecture
 - Sections 4.7-4.10

