

CPE201

Digital Design

By Benjamin Haas

Class 25: Counter Design




Outline

- Designing Counters
 - Examples
- System Design Example



Design

 - Step 1 - Create state machine
 - For counters, the state is the output
- Ex: 3-bit gray code counter




Design

- Step 2 – Next state table

Next-state table for 3-bit Gray code counter.

Present State			Next State		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0
0	0	0	0	0	1
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1
1	1	1	1	0	1
1	0	1	1	0	0
1	0	0	0	0	0

 

Design

- Step 3 – Map state transitions to circuit inputs

Next-state table for 3-bit Gray code counter.

Present State			Next State		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0
0	0	0	0	0	1
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1
1	1	1	1	0	1
1	0	1	1	0	0
1	0	0	0	0	0

this case

Transition table for a J-K flip-flop.

Output Transitions		Flip-Flop Inputs	
Q_N		Q_{N+1}	
0	→	0	J K
0	→	1	0 X
1	→	0	1 X
1	→	1	X 1
			X 0

Q_N : present state

Q_{N+1} : next state

X: “don’t care”

Design

- Step 3b – Table of inputs to create next

J_0	K_0	Q_2	Q_1	Q_0	Q_0 next
1	X	0	0	0	1
X	0	0	0	1	1
X	1	0	1	1	0
0	X	0	1	0	0
1	X	1	1	0	1
X	0	1	1	1	1
X	1	1	0	1	0

Transition table for a J-K flip-flop.

Output Transitions			Flip-Flop Inputs	
Q_N		Q_{N+1}	J	K
0	→	0	0	X
0	→	1	1	X
1	→	0	X	1
1	→	1	X	0

Q_N : present state







Q_{N+1} : next state

X: “don’t care”



Design

      - Step 4 – Karnaugh Maps
 - JK FFs are ACTIVE HIGH, so



J_0	K_0	Q_2	Q_1	Q_0	Q_0 next
1	X	0	0	0	1
X	0	0	0	1	1
X	1	0	1	1	0
0	X	0	1	0	0
1	X	1	1	0	1
X	0	1	1	1	1
X	1	1	0	1	0

Design

- Step 5 – Logical Expressions

$$J_0 = Q_2 Q_1 + \bar{Q}_2 \bar{Q}_1 = \overline{Q_2 \oplus Q_1}$$

$$K_0 = Q_2 \bar{Q}_1 + \bar{Q}_2 Q_1 = Q_2 \oplus Q_1$$

$$J_1 = \bar{Q}_2 Q_0$$

$$K_1 = Q_2 Q_0$$

$$J_2 = Q_1 \bar{Q}_0$$

$$K_2 = \bar{Q}_1 \bar{Q}_0$$

		Q_0	
		0	1
$Q_2 Q_1$	00	0	0
	01	1	0
	11	X	X
	10	X	X

J_2 map

$Q_1 \bar{Q}_0$

		Q_0	
		0	1
$Q_2 Q_1$	00	0	1
	01	X	X
	11	X	X
	10	0	0

J_1 map

$\bar{Q}_2 Q_0$

		Q_0	
		0	1
$Q_2 Q_1$	00	1	X
	01	0	X
	11	1	X
	10	0	X

J_0 map

$\bar{Q}_2 \bar{Q}_1$

$Q_2 Q_1$

		Q_0	
		0	1
$Q_2 Q_1$	00	X	X
	01	X	X
	11	0	0
	10	1	0

K_2 map

$\bar{Q}_1 \bar{Q}_0$

		Q_0	
		0	1
$Q_2 Q_1$	00	X	X
	01	0	0
	11	0	1
	10	X	X

K_1 map

$Q_2 Q_0$

		Q_0	
		0	1
$Q_2 Q_1$	00	X	0
	01	X	1
	11	X	0
	10	X	1

K_0 map

$\bar{Q}_2 Q_1$

$Q_2 \bar{Q}_1$

Design

- Step 6 - Implementation

$$J_0 = Q_2Q_1 + \overline{Q_2}\overline{Q_1} = \overline{Q_2 \oplus Q_1}$$


$$K_0 = Q_2\overline{Q_1} + \overline{Q_2}Q_1 = Q_2 \oplus Q_1$$

$$J_1 = \overline{Q_2}Q_0$$

$$K_1 = Q_2Q_0$$


$$J_2 = Q_1\overline{Q_0}$$

$$K_2 = \overline{Q_1}\overline{Q_0}$$

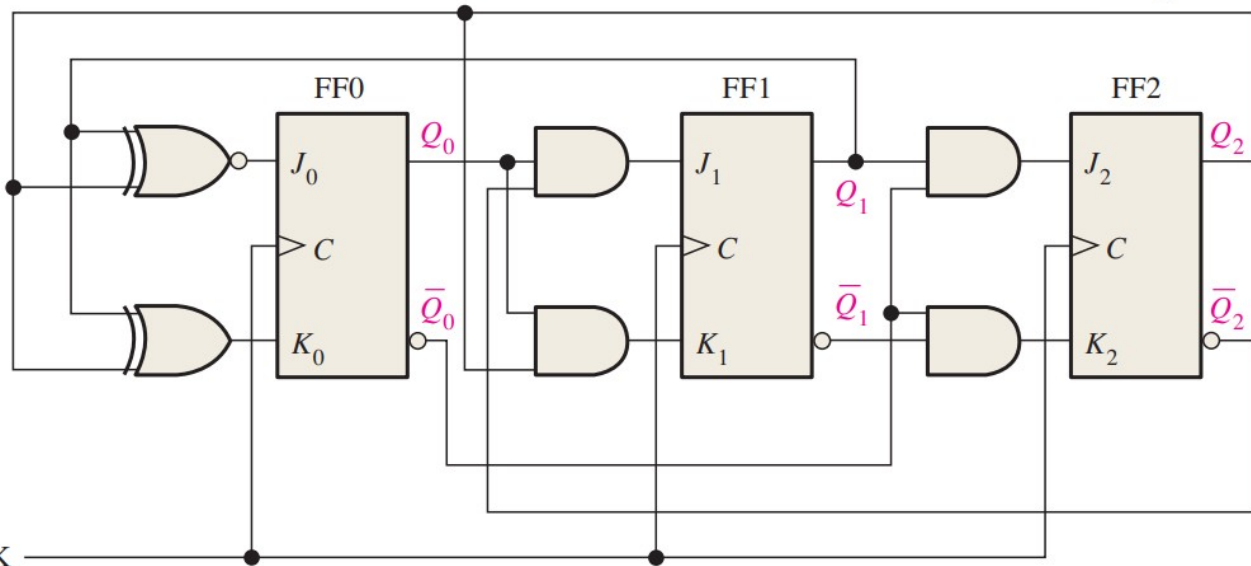

 Example

- 3-bit irregular counter
 - State machine given (step
 - Implement with D FFs




Example

- Step 2 – next state table

Next-state table.

Present State			Next State		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0
0	0	1	0	1	0
0	1	0	1	0	1
1	0	1	1	1	1
1	1	1	0	0	1

 

Example

- Step 3b - Table of inputs to create next

Transition table for a D flip-flop.

Output Transitions			Flip-Flop Input
Q_N		Q_{N+1}	D
0	→	0	0
0	→	1	1
1	→	0	0
1	→	1	1




D_0	Q_2	Q_1	Q_0	Q_0 next
0	0	0	1	0
1	0	1	0	1
1	1	1	1	1
1	0	0	1	1



Example

- Step 4 Karnaugh Maps
 - Pink X's are Don't Care because the state is not in the state machine
 - D FFs are ACTIVE HIGH, so SOP

D_0	Q_2	Q_1	Q_0	Q_0 next
0	0	0	1	0
1	0	1	0	1
1	1	1	1	1

   




Example

- Step 5 – Logical Expressions

$$D_0 = \bar{Q}_0 + Q_2$$

$$D_1 = \bar{Q}_1$$

$$D_2 = \bar{Q}_0 + Q_2\bar{Q}_1$$

   


Example

- Step 6 - Implementation

$$D_0 = \overline{Q_0} + Q_2$$


$$D_1 = \overline{Q_1}$$

$$D_2 = \overline{Q_0} + Q_2\overline{Q_1}$$

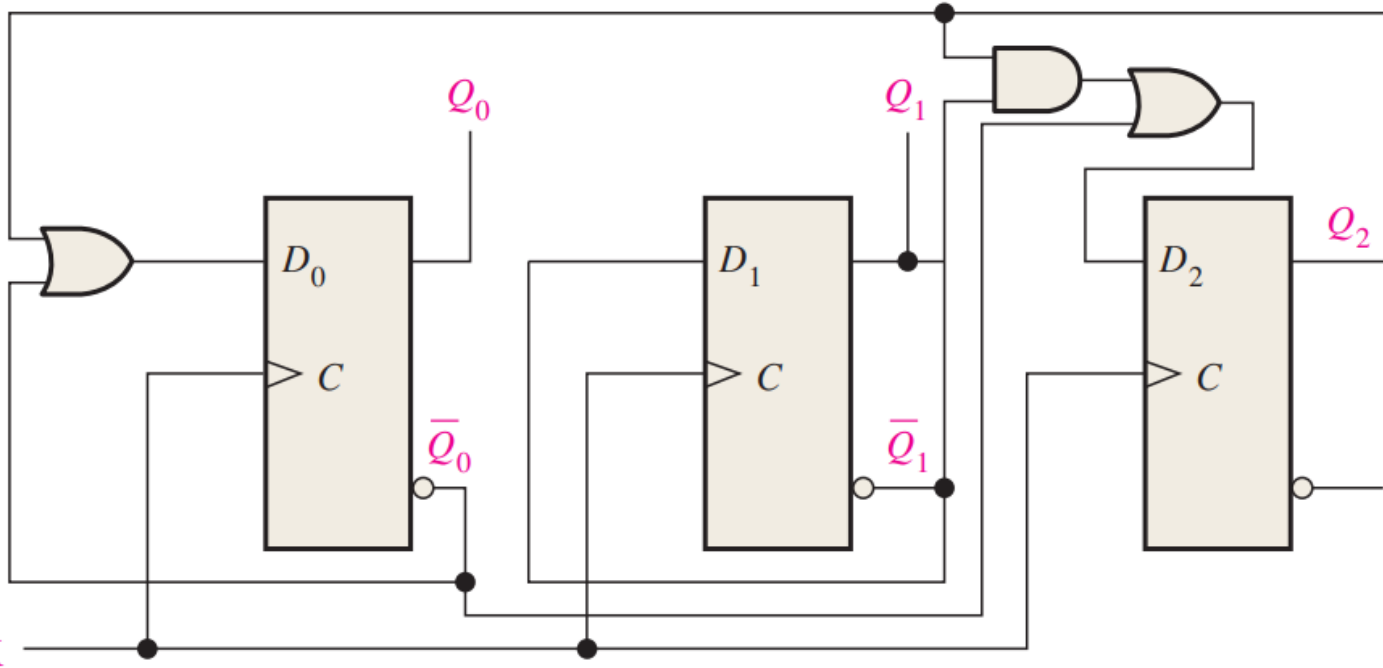


Example 2

- 3-bit Gray Code up/down counter
 - State machine given (step 1)
 - Implement with JK FFs

 

Example 2

- Step 2 – Next state table

 

Next-state table for 3-bit up/down Gray code counter.

Present State			Next State					
			Y = 0 (DOWN)			Y = 1 (UP)		
			Q ₂	Q ₁	Q ₀	Q ₂	Q ₁	Q ₀
0	0	0	1	0	0	0	0	1
0	0	1	0	0	0	0	1	1
0	1	1	0	0	1	0	1	0
0	1	0	0	1	1	1	1	0
1	1	0	0	1	0	1	1	1
1	1	1	1	1	0	1	0	1
1	0	1	1	1	1	1	0	0
1	0	0	1	0	1	0	0	0

$Y = \text{UP/DOWN control input.}$


Example 2

- Consider the up/down' bit to be part of the state

	Present State				Next State		
	Y	Q_2	Q_1	Q_0	Q_2	Q_1	Q_0
$Y = 0$ (DOWN)	0	0	0	0	1	0	0
	0	0	0	1	0	0	0
	0	0	1	1	0	0	1
	0	0	1	0	0	1	1
$Y = 1$ (UP)	0	1	1	0	0	1	0
	0	1	1	1	1	1	0
	0	1	0	1	1	1	1
	0	1	0	0	1	0	1
	1	0	0	0	0	0	1
	1	0	0	1	0	1	1
	1	0	1	1	0	1	0
	1	0	1	0	1	1	0
	1	1	1	0	1	1	1
	1	1	1	1	1	0	1
	1	1	0	1	1	0	0
	1	1	0	0	0	0	0

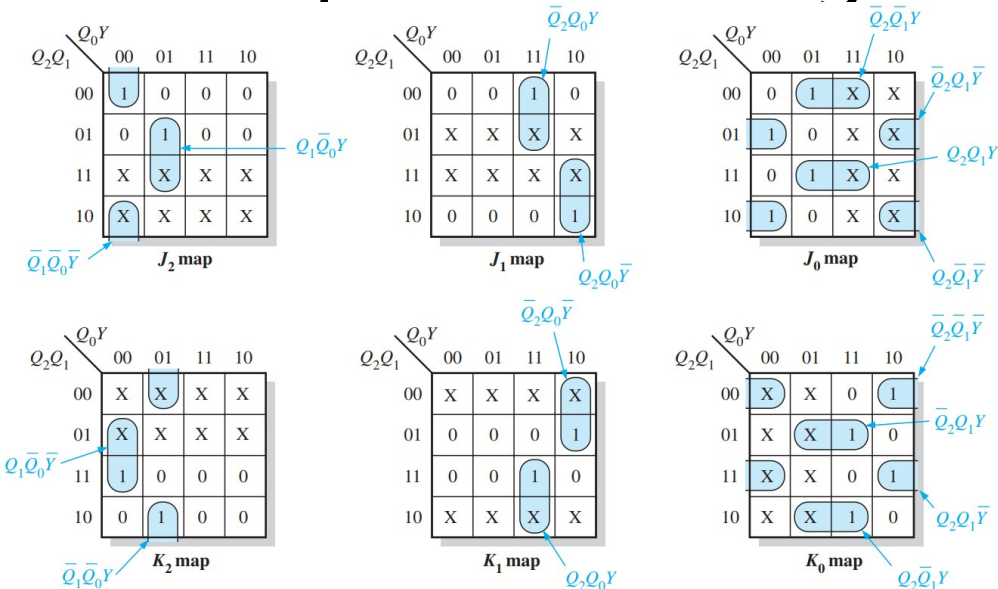Example 2

- Step 3b – Same process as before
- Step 4 – Karnaugh Maps for 4 inputs



Step 5 and Step 6
are the same
process as before

Traffic Signal Design

- Lights at a busy road perpendicular to a side street
- Requirements:
 - Green light on main for at least 25s before a change
 - Green light on side street as long as there are vehicles, up to 25s max
 - Yellow for 4s on both streets




Traffic Signal Design

- Inputs:
 - Vehicle sensor input (1 = vehicle present)
 - System clock (1Hz)
- Outputs:
 - Red, yellow, green signals for both streets (1 = on)



Traffic Signal Design

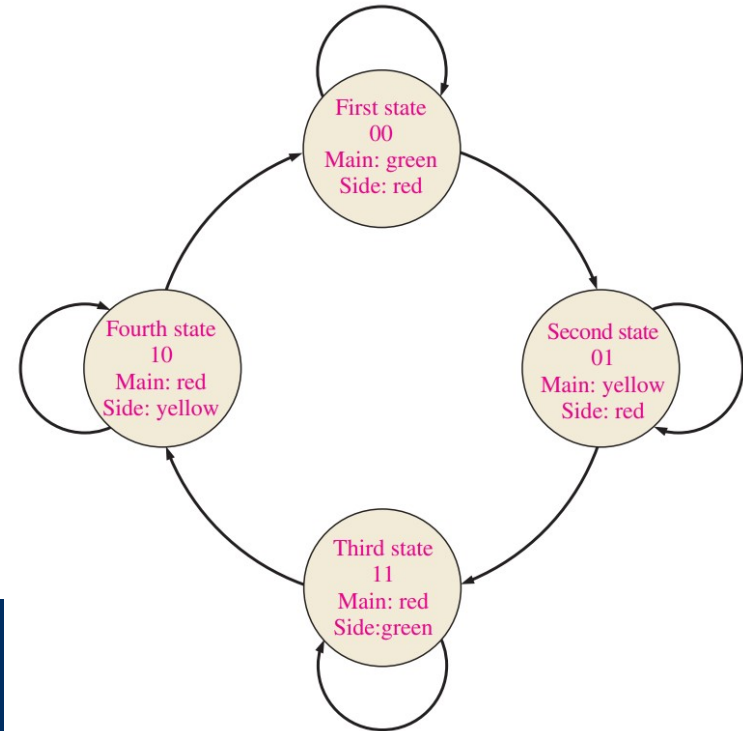- Basic state machine
 - You know how traffic lights work
 - Also added gray code to represent each state as a number



Traffic Signal Design

- Let's describe the transitions
 - First state is 'normal', takes a vehicle on side street and 25s to have passed to change to next state
 - Second state, wait for 4s on yellow
 - Third state, stay here as long as a vehicle is present and it is less than 25s in this state
 - Fourth state, same as second state




Traffic Signal Design

- Now make some inputs/variables for the state machine
 - Make from state transitions, make vars binary
 - V_s = vehicle present on side street
 - T_L = long timer (25s) is on
 - T_s = short timer (4s) is on



Traffic Signal Design

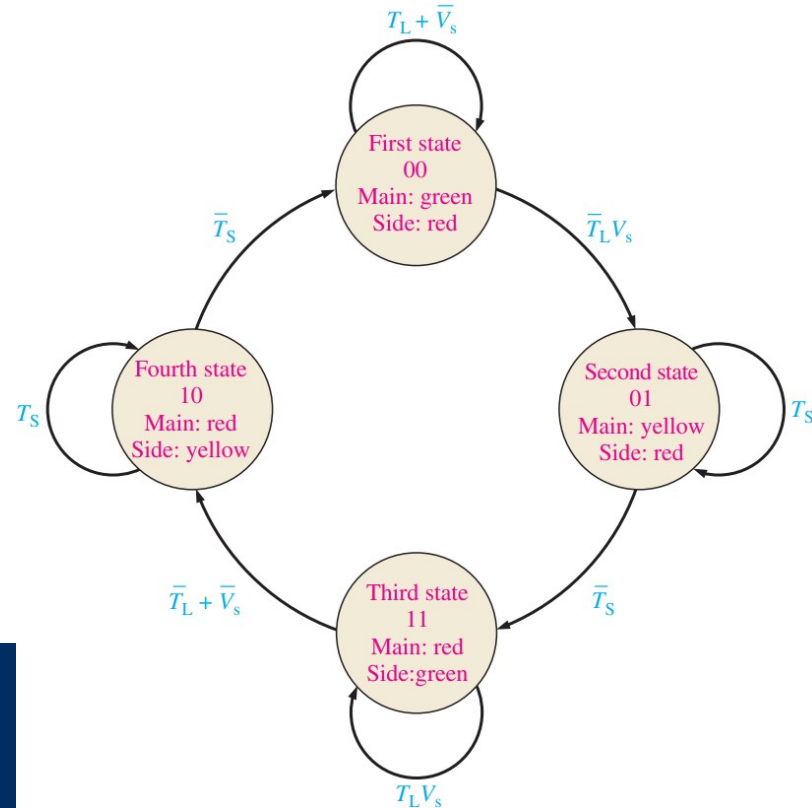- Note that each transition condition is literally the NOT of the looping condition




Traffic Signal Design

- The controller can be broken into several parts
 - Sequential logic - takes in all inputs on state machine and outputs state gray code
 - Combinational Logic – decodes state, triggers timers, and creates light outputs
 - Timers – input triggers and clock, outputs for if each timer is running (creates T_L and T_S)




Traffic Signal Design

 - Break each block down until it does one thing
 - Sequential is co
 - Timers
 - Combination st
 - does too much



Traffic Signal Design

 - Do your thinking in blocks to simplify problems
 - State decoder – current state is 110011
 - State directly ties to light colors and starts a timer




Traffic Signal Design

- State decoder from truth table

Truth table for the state decoder.

State Inputs (Gray Code)		State Outputs			
G_1	G_0	S_1	S_2	S_3	S_4
0	0	1	0	0	0
0	1	0	1	0	0
1	1	0	0	1	0
1	0	0	0	0	1

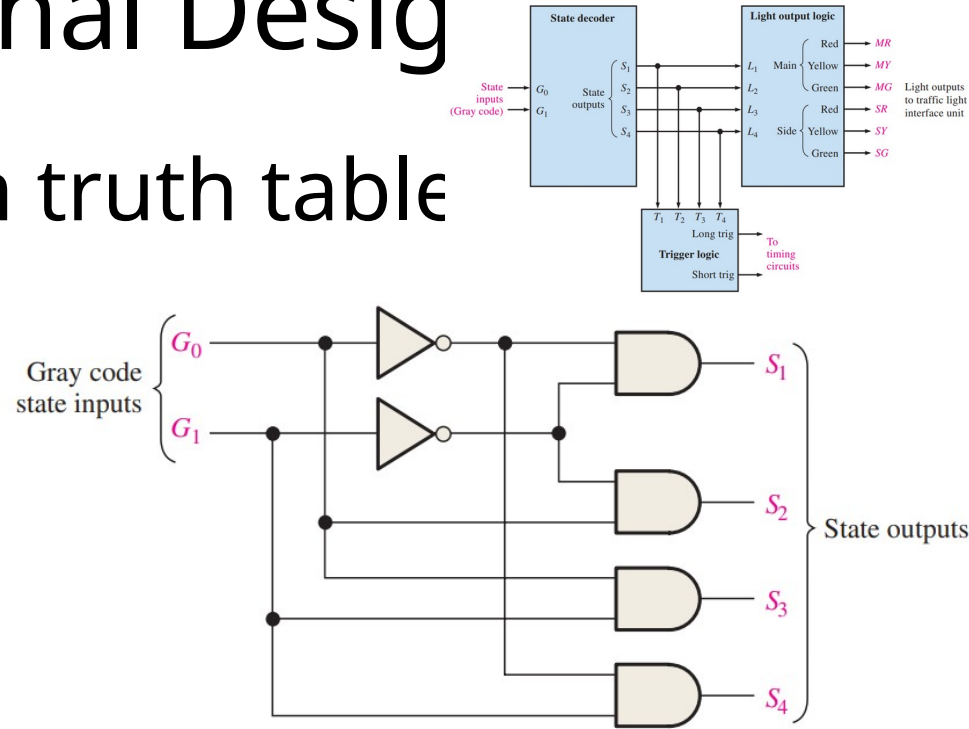

Traffic Signal Design

- Inputs/Outputs are not usually named the same

- $MR = L3 + L4$




- $MY = L2$

- $MG = L1$

- $SR = L1 + L2$




- $SY = L4$

- $SG = L3$

   



Traffic Signal Design

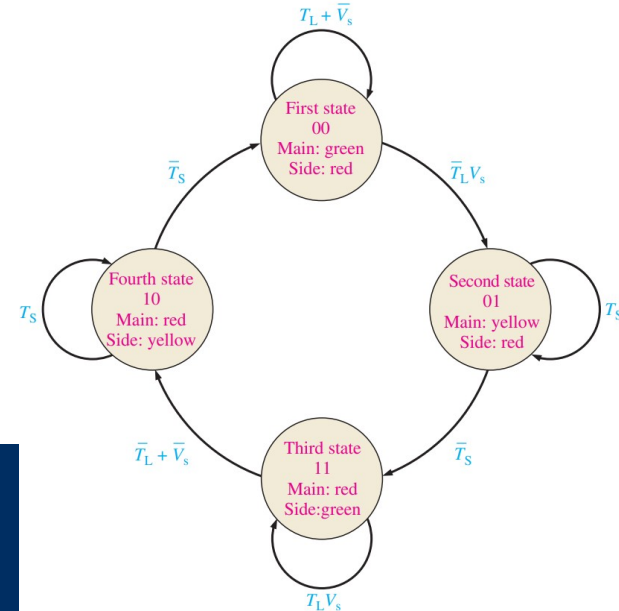  - S1 and S3 start long timer
- S2 and S4 start short timer



Traffic Signal Design

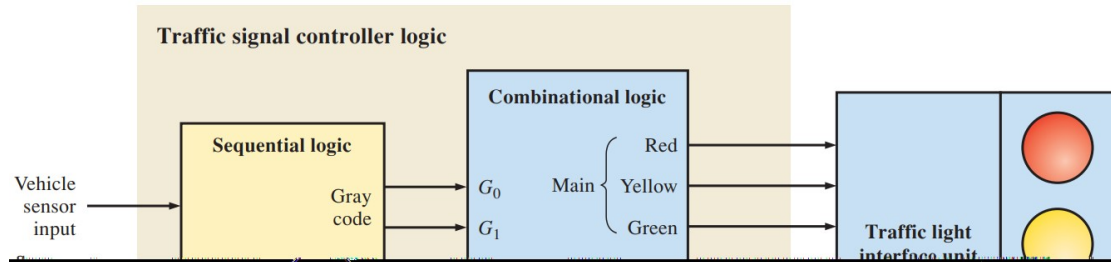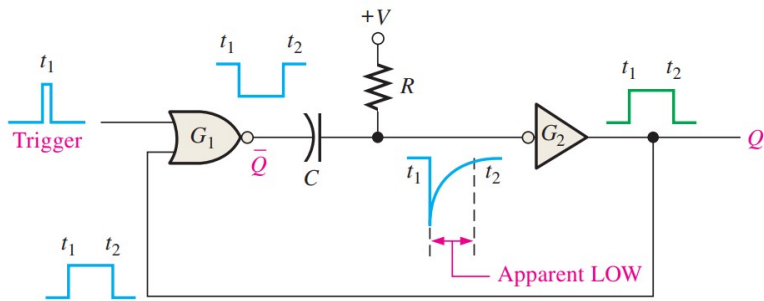- TS and TL are high when timer is running, just like a one shot




Traffic Signal Design

- $t_W = 0.7RC$
- $4s = 0.7R_{4s}C_{4s}$
- If $C_{4s} = 1000\mu\text{F}$, then $R_{4s} = 5,714\Omega$
- $25s = 0.7R_{25s}C_{25s}$
- If $C_{25s} = 1000\mu\text{F}$, then $R_{25s} = 35,714\Omega$





Traffic Signal Design

- One chunk left, it's a 2-bit counter

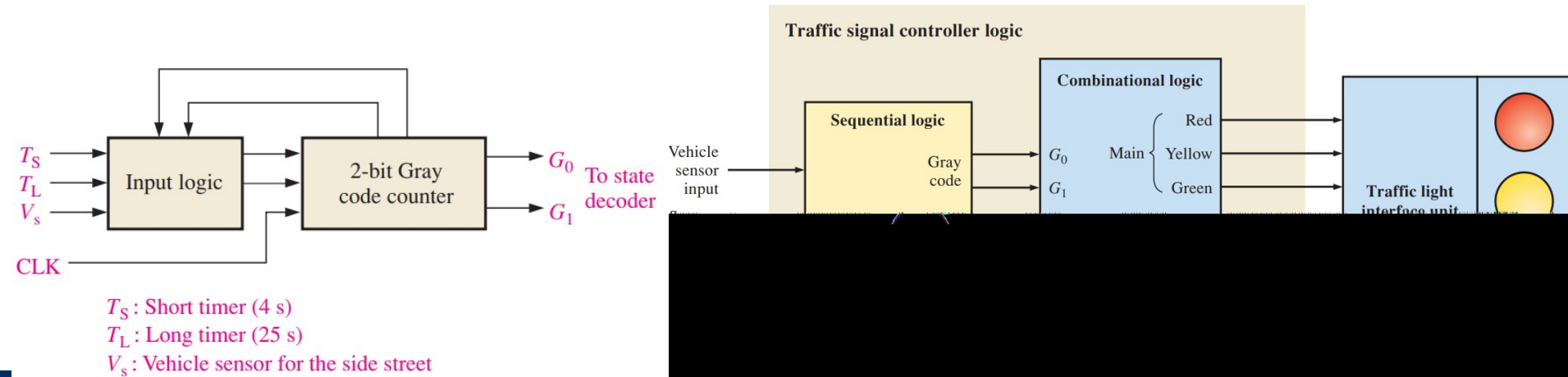


Traffic Signal Design

 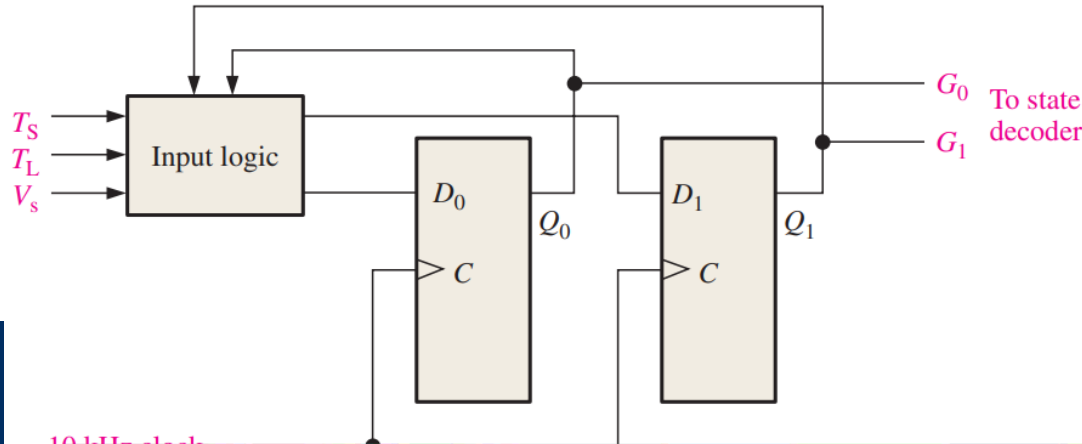- We'll use D FFs
 - Arbitrarily pick system clock at 10kHz
 - Step 1 - State machine is given



Traffic Signal Design

- Step 2- Next state table

 

Traffic Signal Design

- Karnaugh maps would be very complicated with 5 variables (G_1 , G_0 , V_S , T_L , T_S)
 - Also a sparse table, so you can opt to not simplify the circuit to be quick
 - Write out the terms that make $D_0 = 1$




Traffic Signal Design

- $D_0 = G_1 G_0' T_L' V_S + G_1 G_0' T_S + G_1 G_0 T_S' + G_1 G_0 T_L V_S$
- $D_1 = G_1' G_0 T_S' + G_1 G_0' T_S$

Traffic Signal Design

- That's all the pieces!

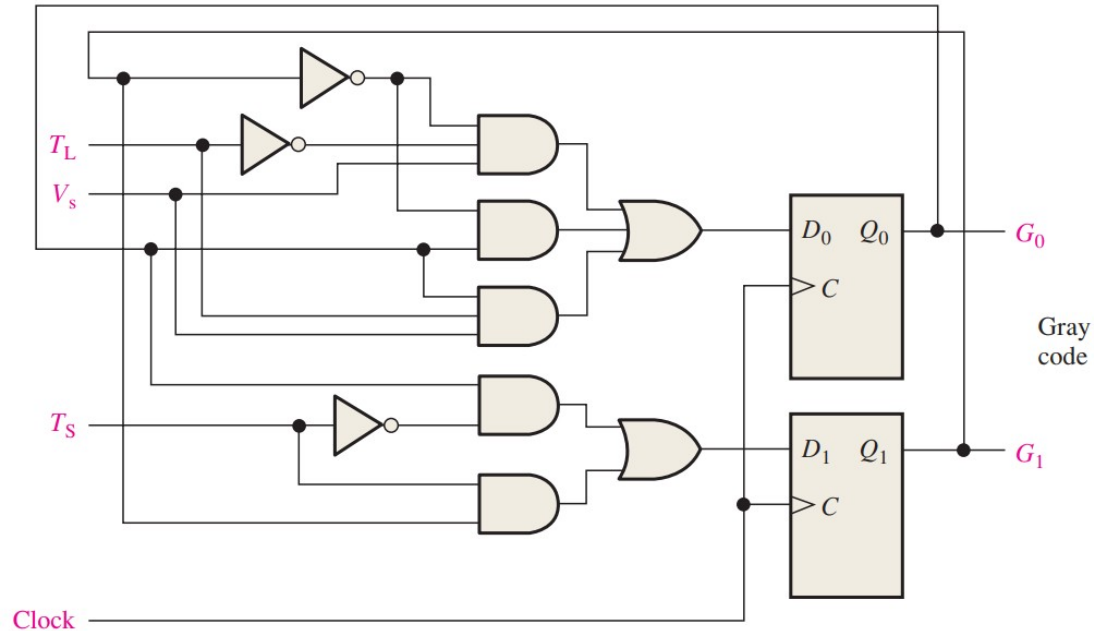

Reading

- This lecture
 - 9.5, Ch6 and Ch7 Applied Logic
- Next lecture
 - Sections 12.1-12.3

