

Answer all questions completely. Put a box around the final solution. Put your name on it. Show your work.

1. Convert the following binary number to floating point format. Give your answer as 4 hexadecimal bytes. (20 points)

-11011101.0001010001011111001

2. Given the combinational logic circuit in Figure 1:
 - a. Give the Boolean expression for 1, 2, 3, 4, and the Output. (20 points)
 - b. Complete the truth table for the circuit. (40 points)

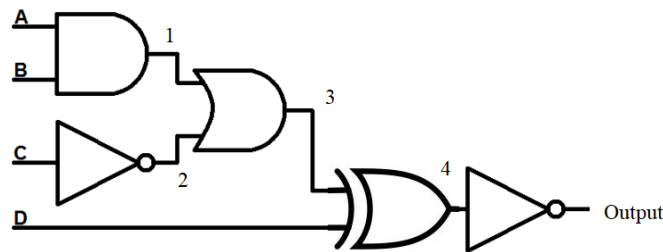


Figure 1

A	B	C	D	1	2	3	4	Output
0	0	0	0					
0	0	0	1					
0	0	1	0					
0	0	1	1					
0	1	0	0					
0	1	0	1					
0	1	1	0					
0	1	1	1					
1	0	0	0					
1	0	0	1					
1	0	1	0					
1	0	1	1					
1	1	0	0					
1	1	0	1					
1	1	1	0					
1	1	1	1					

3. Determine the minimum SOP expression for the Karnaugh map in Figure 2. (20 points)

<i>AB</i> \ <i>CD</i>	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	0	0	1	0
10	1	0	0	1

Figure 2